




Application Note 2004-4a

SensComp, Inc.
36704 Commerce Rd.
Livonia, MI 48150
Telephone: (734) 953-4783
Fax: (734) 953-4518
www.senscomp.com

Connecting Relays to the MINI-S Ultrasonic Sensor

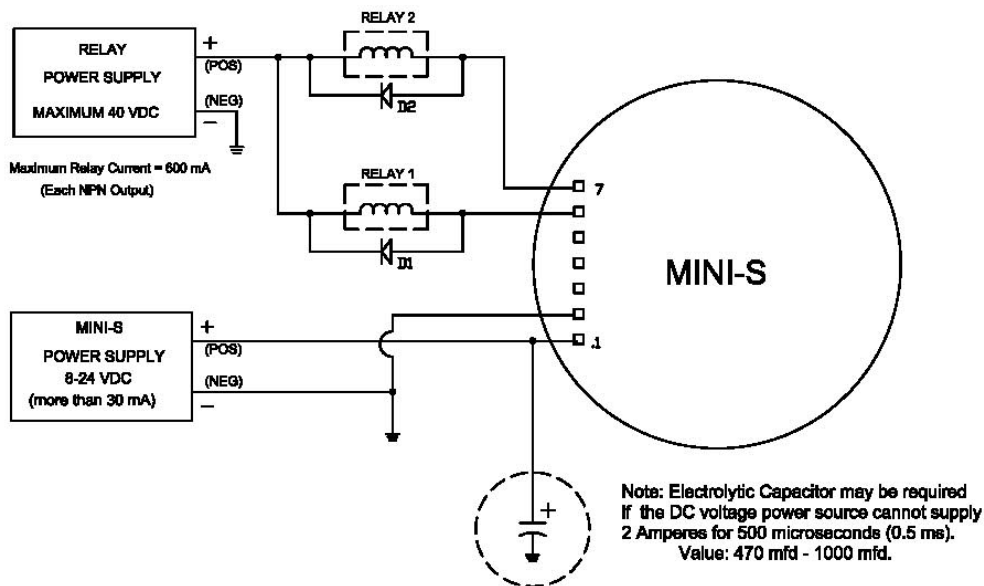The Figure below shows the basic connections needed for the Mini-S Ultrasonic Sensor to turn on and off relays at two different set-point distances.



Either two separate power supplies, one for the relays and one for the MINI-S power, can be used. Or a single 12 VDC (or a 24 VDC) power supply could be used for both the Sensor and the relays (such as for using a 12 VDC, or a 24 VDC, relay).

Relay 1 and Relay 2 can be any DC relay consuming a current of less than 600mA. The relay coil voltage can be up to +40 VDC maximum.

Diodes D1 and D2 prevent relay coil reverse voltage flow into the Mini-S when power is removed from the relay coils. A typical diode used is a 1N4002 or equivalent.

